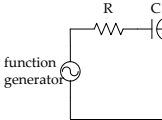


stub simulating
expected input

stub simulating
expected output



function
generator

R

C

BJT Amplifier

R_L