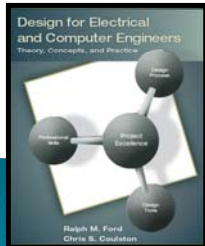


## Chapter 5 – Functional Decomposition




---

---

---

---

---

---

---

---

## Time for DESIGN!



Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

---

---

---

---

---

---

---

---

## Motivation – System Design

Team of engineers who build a system need:

- ▶ An abstraction of the system
- ▶ An unambiguous communication medium
- ▶ A way to describe the subsystems
  - Inputs
  - Outputs
  - Behavior
- ▶ Functional Decomposition
  - Function – transformation from inputs to outputs
  - Decomposition – reduce to constituent parts

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

---

---

---

---

---

---

---

---

## Learning Objectives

By the end of this chapter, you should:

- ▶ Understand the differences between bottom-up and top-down design.
- ▶ Know what functional decomposition is and how to apply it.
- ▶ Be able to apply functional decomposition to different problem domains.
- ▶ Understand the concept of coupling and cohesion, and how they impact design.

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

4

---

---

---

---

---

---

---

---

## 5.1 Bottom Up

- ▶ Given constituent parts
- ▶ Develop a working system
  - Build modules to accomplish specific tasks
  - Integrate modules together into working system
- ▶ For example
  - Given a supply AND, OR and NOT gates.
  - Build a computer
- ▶ Pros
  - Leads to efficient subsystem
- ▶ Cons
  - Complexity is difficult to manage
  - Little thought to designing reusable modules
  - Redesign cycles

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

5

---

---

---

---

---

---

---

---

## Top Down

- ▶ Given the specification of a system
- ▶ Develop a working system
  - Divide the problem into abstract modules
  - Reiterate until constituent parts are reached
- ▶ Pros
  - Highly predictable design cycle
  - Efficient division of labor
- ▶ Cons
  - More time spent in planning

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

6

---

---

---

---

---

---

---

---

## 5.2 Functional Decomposition

A mathematical analogy

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

7

---

---

---

---

---

---


---

---
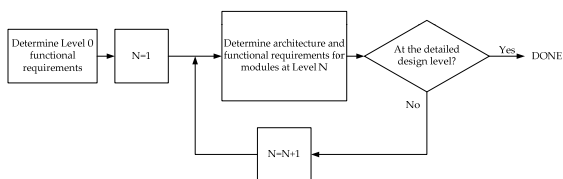
## Functional Decomposition

Recursively divide and conquer

- Split a module into several submodules
- Define the input, output, and behavior
- Stop when you reach realizable components



Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

8

---

---

---

---

---


---

---

---
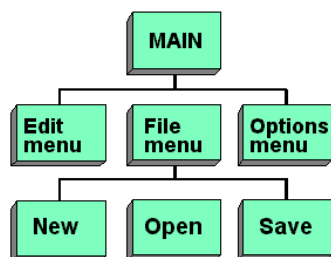
## Example: Program menu

From Computer Desktop Encyclopedia  
© 1998 The Computer Language Co. Inc.



Design for Electrical and Computer Engineers, McGraw Hill  
Copyright 2005 and Chris Coulston, Copyright 2007

9

---

---

---

---

---

---

---

---

### 5.3 Guidance

- The design process is iterative
- Upfront time saves redesign time later
- Submodules should have similar complexity
- Precise input, output, and behavior specifications
- Look for innovation
- Don't decompose *ad infinitum*
- Use suitable abstraction to describe submodules

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

10

---

---

---

---

---

---

---

---

### Guidance, continued

- Look at how it has been done before
- Use existing technology
- Keep it simple
- Communicate results

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

11

---

---

---

---

---

---

---

---

### 5.4 Application: Audio Power Amplifier

The system must

- Accept an audio input signal source with a maximum input voltage of 0.5V peak.
- Have adjustable volume control between zero volume and the maximum volume level.
- Deliver a maximum of 50W to an 8Ω speaker.
- Be powered by a standard 120V 60Hz AC outlet.

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

12

---

---

---

---

---

---

---

---

## Level 0

Module	Audio Power Amplifier
Inputs	Audio input signal: 0.5V peak. Power: 120 volts AC rms, 60Hz. User volume control: variable control.
Outputs	Audio output signal: 2V peak value.
Functionality	Amplify the input signal to produce a 50W maximum output signal. The amplification should have variable user control. The output volume should be variable between no volume and a maximum volume level.



Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

13

---

---

---

---


---

---

---

---

## Level 1

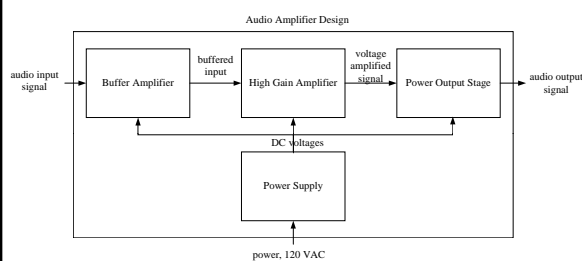

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

14

---

---

---

---

---

---

---

---

## Level 1 – Buffer amp

Module	Buffer Amplifier
Inputs	- Audio input signal: 0.5V peak. - Power: $\pm 25V$ DC.
Outputs	- Audio signal: 0.5V peak.
Functionality	Buffer the input signal and provide unity voltage gain. It should have an input resistance $>1M\Omega$ and an output resistance $<100\Omega$ .

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

15

---

---

---

---

---

---

---

---

## Level 1 – High gain amp

Module	High Gain Amplifier
Inputs	<ul style="list-style-type: none"> <li>- Audio input signal: 0.5V peak.</li> <li>- User volume control: variable control.</li> <li>- Power: <math>\pm 25V</math> DC</li> </ul>
Outputs	<ul style="list-style-type: none"> <li>- Audio signal: 20V peak.</li> </ul>
Functionality	Provide an adjustable voltage gain, between 1 and 40. It should have an input resistance $>100k\Omega$ and an output resistance $<100\Omega$ .

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

16

---

---

---

---

---

---

---

---

## Application Domains

- ▶ Electronics Design
- ▶ Digital Design
- ▶ Software Design
- ▶ See the book for more in-depth examples

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

17

---

---

---

---

---

---

---

---

## 5.7 Example: Thermometer Design

The system must

- ▶ Measure temperature between 0 and 200°C.
- ▶ Have an accuracy of 0.4% of full scale.
- ▶ Display the temperature digitally, including one digit beyond the decimal point.
- ▶ Be powered by a standard 120V 60Hz AC outlet.
- ▶ Use an RTD (thermal resistive device) that has an accuracy of 0.55°C over the range. The resistance of the RTD varies linearly with temperature from 100Ω at 0°C to 178Ω at 200°C.

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

18

---

---

---


---

---

---

---

---

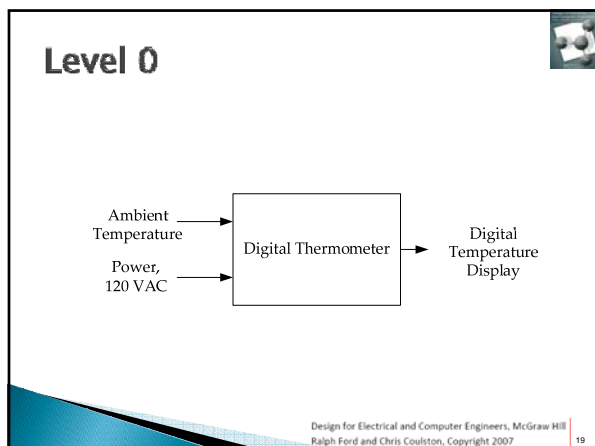


---

---

---

---

---

---

---

---

## Level 0

<i>Module</i>	Digital Thermometer
<i>Inputs</i>	<ul style="list-style-type: none"> <li>- Ambient temperature: 0-200°C.</li> <li>- Power: 120V AC power.</li> </ul>
<i>Outputs</i>	<ul style="list-style-type: none"> <li>- Digital temperature display: A four digit display, including one digit beyond the decimal point.</li> </ul>
<i>Functionality</i>	Displays temperature on digital readout with an accuracy of 0.4% of full scale.

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

---

---

---


---

---

---

---

---

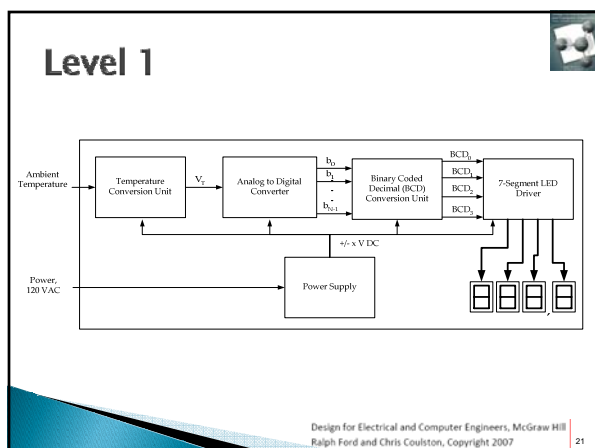


---

---

---

---

---

---

---

---

## Level 1

<i>Module</i>	Temperature Conversion Unit
<i>Inputs</i>	<ul style="list-style-type: none"> <li>- Ambient temperature: 0-200°C.</li> <li>- Power: 2V DC (to power the electronics).</li> </ul>
<i>Outputs</i>	<ul style="list-style-type: none"> <li>- <math>V_T</math>: temperature proportional voltage. <math>V_T = \alpha T</math>, and ranges from 2 to 2V.</li> </ul>
<i>Functionality</i>	Produces an output voltage that is linearly proportional to temperature. It must achieve an accuracy of 2%.

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

22

---

---

---

---

---

---

---

---

## Level 1

<i>Module</i>	A/D Converter
<i>Inputs</i>	<ul style="list-style-type: none"> <li>- <math>V_T</math>: voltage proportional to temperature that ranges from 2 to 2V.</li> <li>- Power: 2V DC.</li> </ul>
<i>Outputs</i>	<ul style="list-style-type: none"> <li>- <math>b_{N-1} \dots b_0</math>: 2-bit binary representation of <math>V_T</math>.</li> </ul>
<i>Functionality</i>	Converts analog input to binary digital output.

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

23

---

---

---

---

---

---

---

---

## Design Details

- How would you determine the unknown details in the previous 2 slides?

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

24

---

---

---

---

---

---

---

---



## 5.8 Coupling and Cohesion

- ▶ What is coupling?
- ▶ How much coupling is there in the modules in the Level 1 of the previous amplifier example?
- ▶ Phenomena of highly coupled systems
  - A failure in 1 module propagates
  - Difficult to redesign 1 module
- ▶ Phenomena of low coupled systems
  - Discourages reutilization of a module

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

25

---

---

---

---

---

---

---

---

## Cohesion

- ▶ What is cohesion?
- ▶ Phenomena of highly cohesive systems
  - Easy to test modules independently
  - Simple (non-existent) control interface
- ▶ Phenomena of low cohesive systems
  - Less reuse of modules

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

26

---

---

---

---

---

---

---

---

## 5.9 Project Application: The Functional Design

- ▶ **Design Level 0**
  - Present a single module block diagram with inputs and outputs identified.
  - Present the functional requirements: inputs, outputs, and functionality.
- ▶ **Design Level 1**
  - Present the Level 1 diagram (system architecture) with all modules and interconnections shown.
  - Describe the theory of operation. This should explain how the modules work together to achieve the functional objectives.
  - Present the functional requirements for each module at this level.
- ▶ **Design Level N (for N>1)**
  - Repeat the process from design Level 1 as necessary.
- ▶ **Design Alternatives**
  - Describe the different alternatives that were considered, the tradeoffs, and the rationale for the choices made. This should be based upon concept evaluation methods in Chapter 4.

Design for Electrical and Computer Engineers, McGraw Hill  
Ralph Ford and Chris Coulston, Copyright 2007

27

---

---

---

---

---

---

---

---

## 5.10 Summary



- Design approach: top-down and bottom-up
- Functional Decomposition
  - Iterative decomposition
  - Input, output, and function
  - Applicable to many problem domains
- Coupling – interconnectedness of modules
- Cohesion – focus of modules

Design for Electrical and Computer Engineers, McGraw-Hill  
Ralph Ford and Chris Coulston, Copyright 2007

28

---

---

---

---

---

---

---

---